

# QUIC

Intro to quantum information + computation  
through  
Classical + quantum addition

# Classical addition

$a = 7$

$b = 4$

$$\begin{array}{r} 1 \\ 7 \\ + 4 \\ \hline 11 \end{array}$$

Sum  
Carry

Q: How do computers represent #s?

$$\begin{array}{r} a = 7 = \begin{array}{ccc} 2^2 & 2^1 & 2^0 \\ \underline{1} & \underline{1} & \underline{1} \end{array} = 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 \\ b = 4 = \begin{array}{ccc} \underline{1} & \underline{0} & \underline{0} \end{array} \end{array}$$

Full adder  
Input: 3 bits  
Output: Sum, Carry

$$\begin{array}{r} 1 \\ 11 \\ + 10 \\ \hline 101 \end{array}$$

Half adder  
Input: 2 bits  
Output: Sum, Carry

Q: How do computers perform op's?

# Operations

NOT

a	NOT a
0	1
1	0

XOR

a	b	a XOR b
0	0	0
0	1	1
1	0	1
1	1	0

AND

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1


SUM

CARRY


AND!

XOR!

$a, b \in \{0, 1\}$

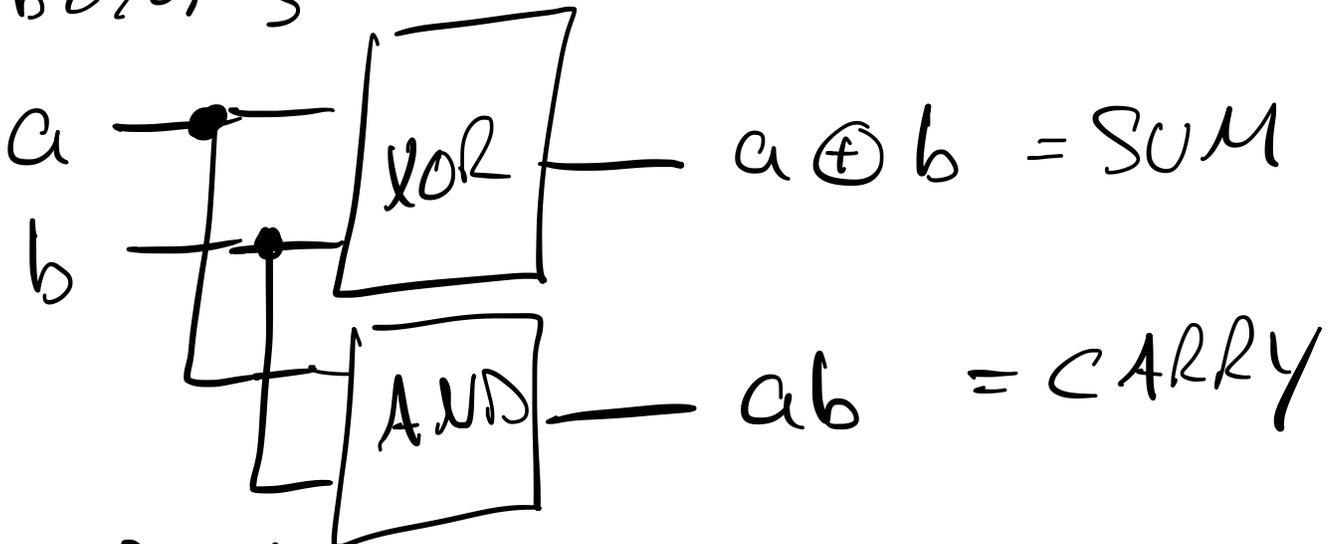

Half adder

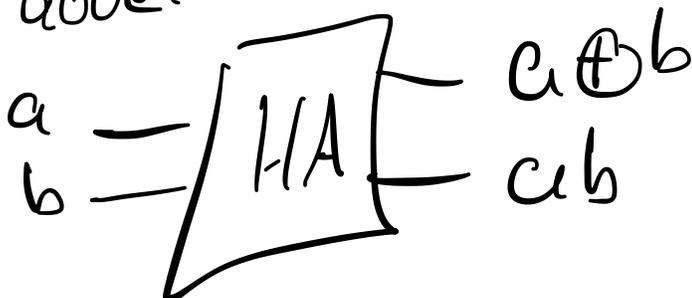

# Full adder

a	b	C <sub>in</sub>	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM} = a \oplus b \oplus C_{in}$$

$$\text{CARRY} = ab \oplus C_{in} (a \oplus b)$$


# Ripple Carry adder

$$a = a_3 a_2 a_1$$

$$b = b_3 b_2 b_1$$

$$a_i \in \{0, 1\}$$

$$b_i \in \{0, 1\}$$

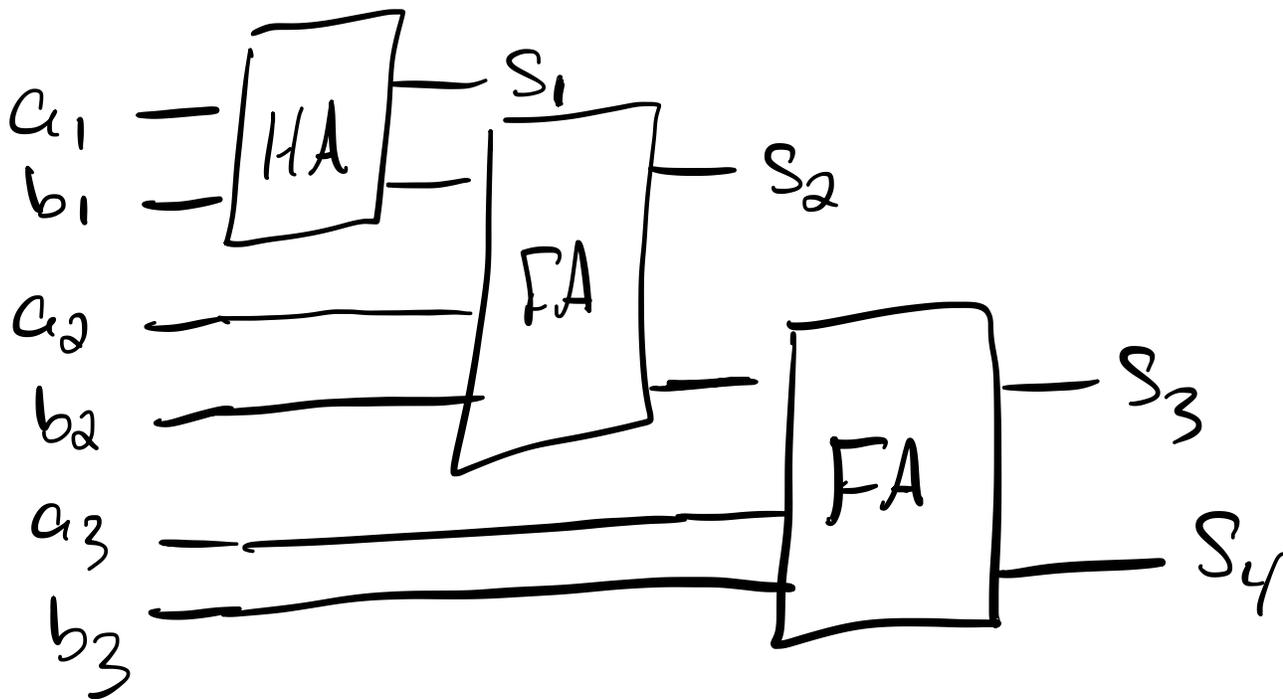

$$S = s_4 s_3 s_2 s_1$$

# Quantum


\* Logic gates (op's) must be reversible (aka unitary)

Can we quantumly do

- FA?
- HA?
- AND?
- XOR?

Input		Output	
a	b	a	$a \oplus b$
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0


CNOT

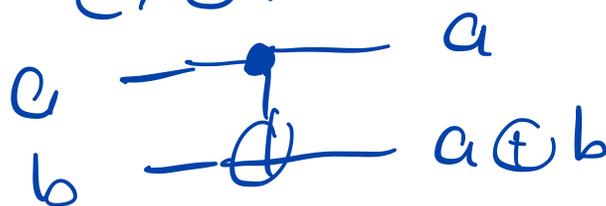




# AND

a	b	a	b	a AND b
0	0	0	0	0
0	1	0	1	0
1	0	1	0	0
1	1	1	1	1

# Toffoli

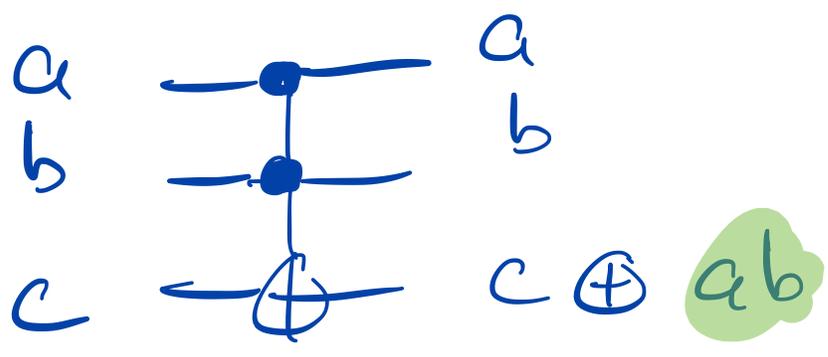

# Quantum Sum

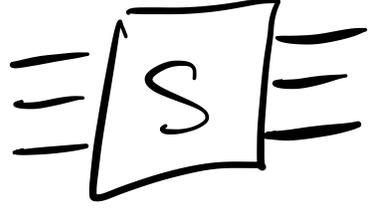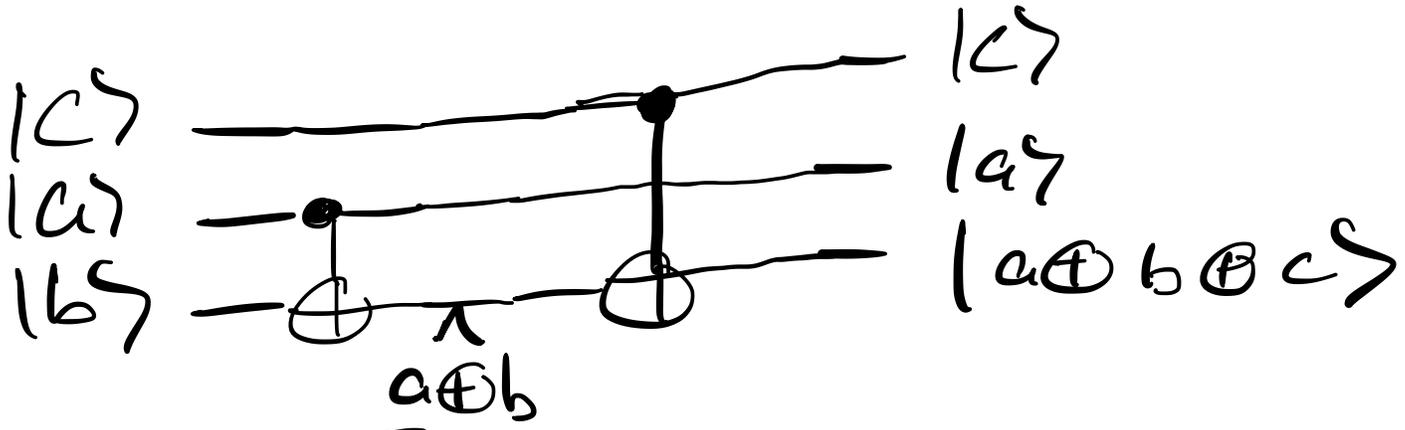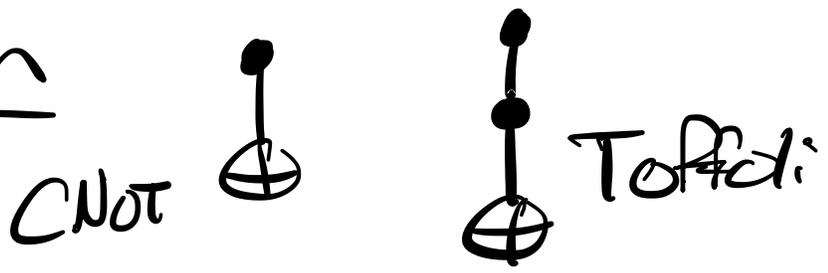

$CARRY = ab \oplus cin(a \oplus b)$

# Quantum Carry

